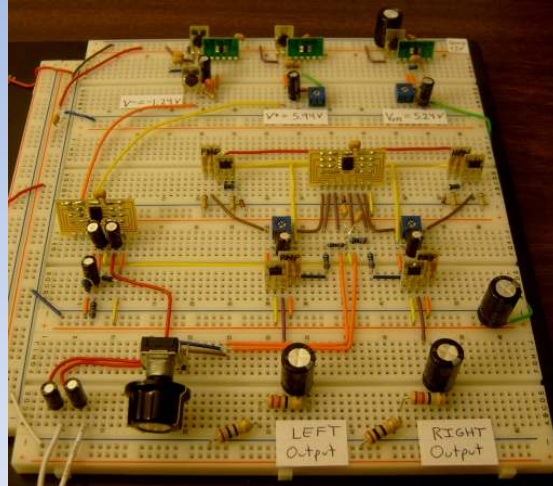


High Efficiency Headphone Amp

EE 410 Design Competition



Devin Ott

Kevin Cheng

Xiangyu Dong

Greg Abrami

Outline

- Design Requirements and Goals
- Design Approach
- Circuit Design
 - Schematic
 - Flowchart
- Experimental Data
- Results Summary
- Conclusion

Purpose and Goals

- Design High Efficiency Headphone Amplifier:

Power Requirements	
Power Consumption	< 400mW
Battery Life	> 90hrs
Noise Requirements	
THD (10mW output)	< 0.1%
THD (100mW output)	< 1.0%
Noise Density (output)	< -128dB/VHz
Material Cost	
Overall	< \$40

Number One Goal



Design Approach

Minimize power consumption

- Minimize supply voltage
 - Load requires $\geq 2.53V_{\text{PEAK}}$
- Minimize currents

$$P = IV$$

Rail-to-Rail Output

- Advantage: lower power consumption
 - Only requires $2 \times 2.53\text{V} = 5.06\text{V}$ supply
- Disadvantage: complexity
 - Difficult to design output stage


CHALLENGE:

Is it possible to attain the efficiency of rail-to-rail output using a simple output stage?

SOLUTION:

Emitter Follower Output Stage

- Keep collector voltages low: $|V_C| = 2.6\text{V}$
- Use low $V_{CE(sat)}$ transistors (BISS)
- Use $\pm 3.4\text{V}$ amplifier circuit to drive V_B


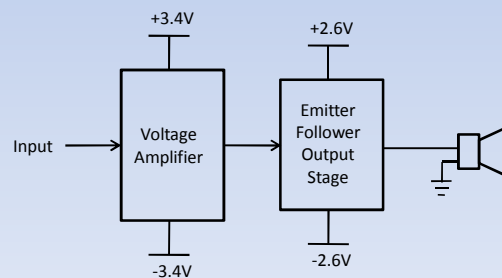


Reduces Power Consumption by approximately $V_{BE} \times I_C \times 2$


BISS (Breakthrough In Small-Signal) Transistor

Very low $V_{CE(sat)} < 100\text{mV}$


High Gain: $h_{FE} \approx 450$

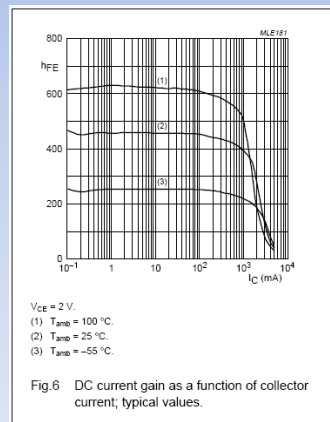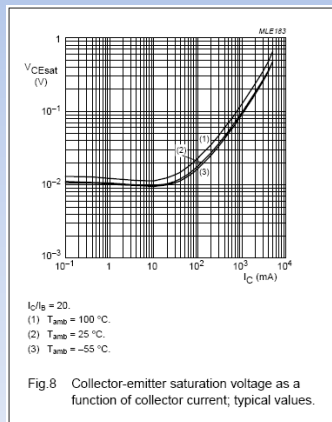


Circuit Diagram

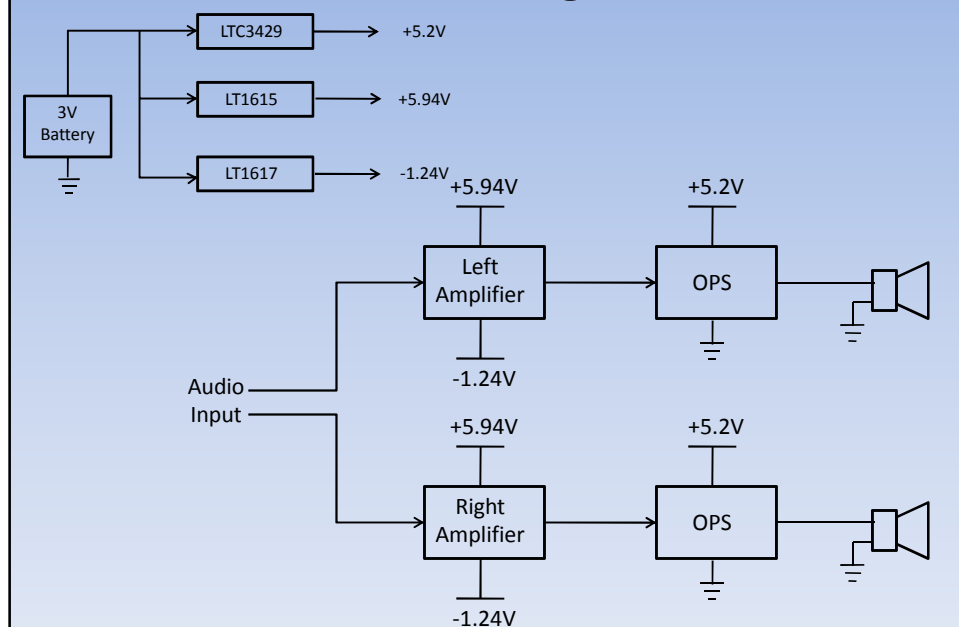


Amplifier Stage

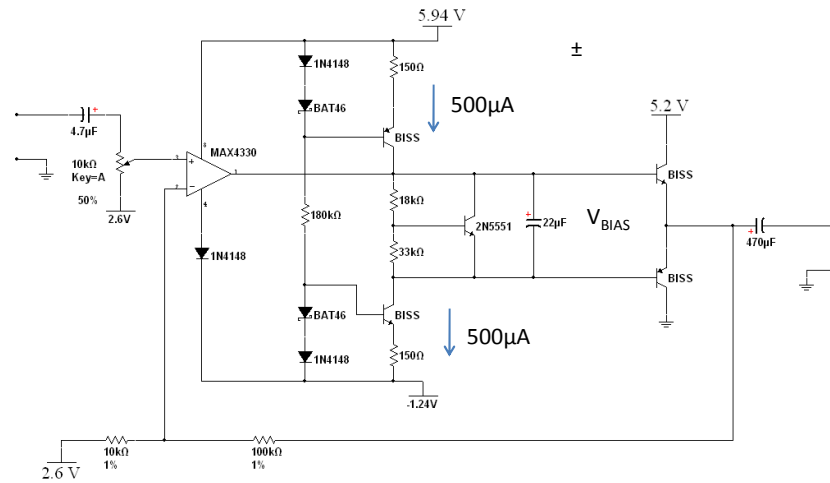


Amplifier Stage

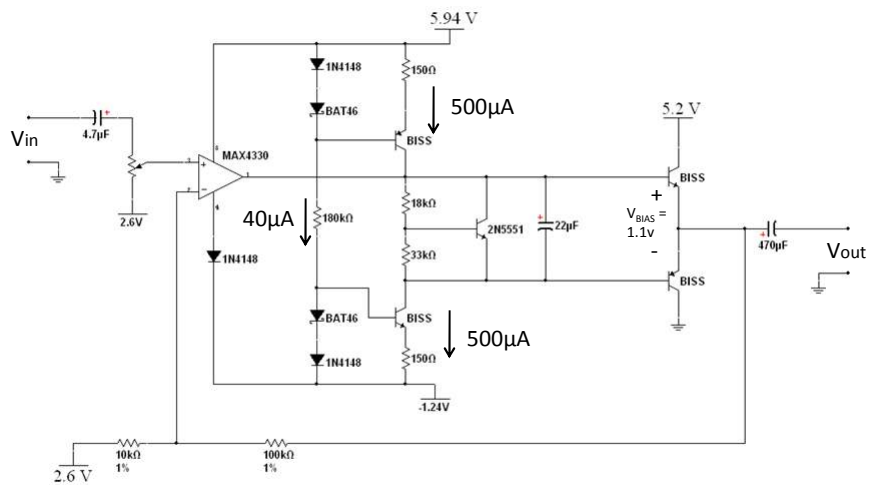



DC/DC Converters

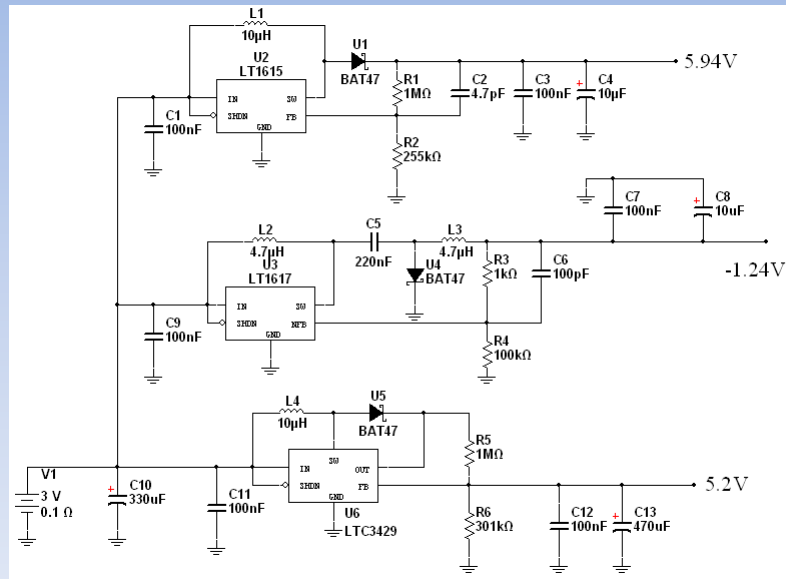

Half Supply Generator


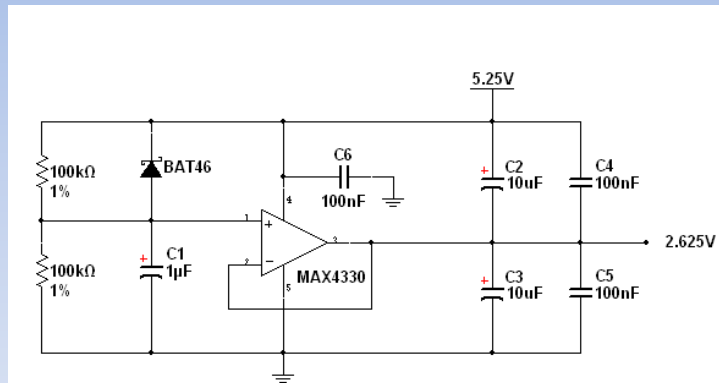


Turn-On Transient

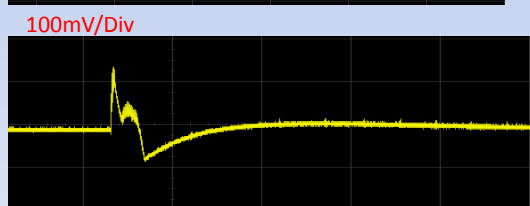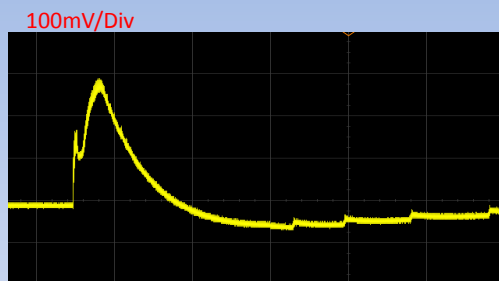


C=4.7uF

Bias Capacitors

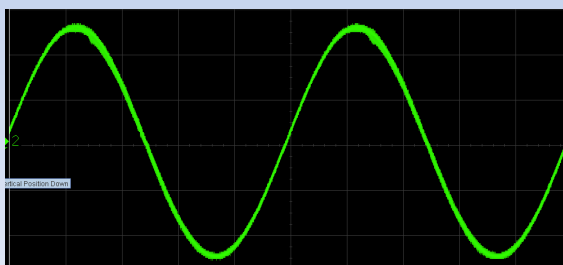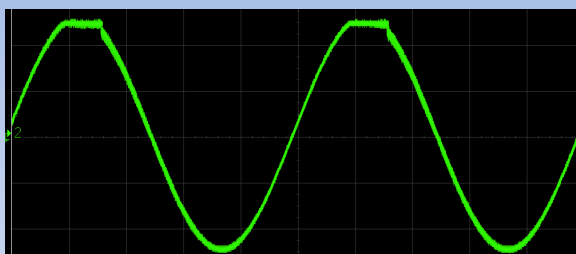



Switching Noise

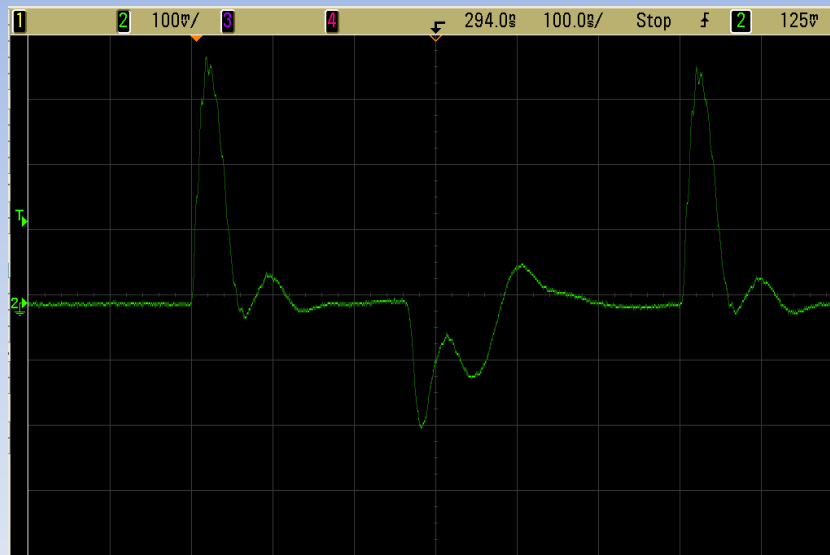


Switching Frequency → 1.67MHz

Crossover Distortion



Vbias= 1.1V

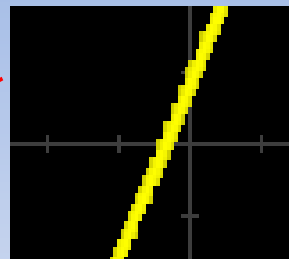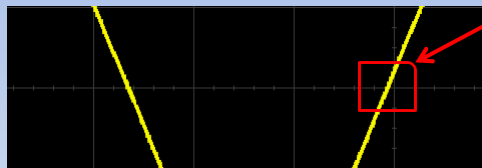


Vbias= 0.6V

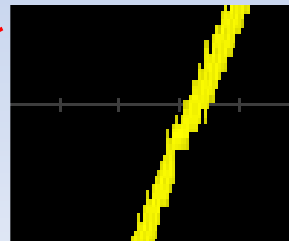

Output at Max Power

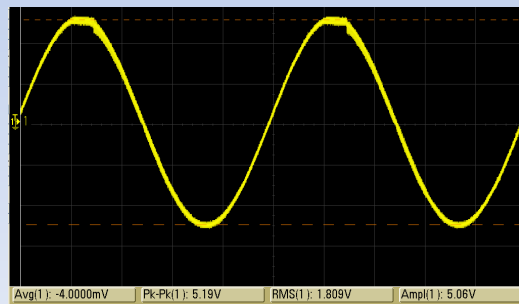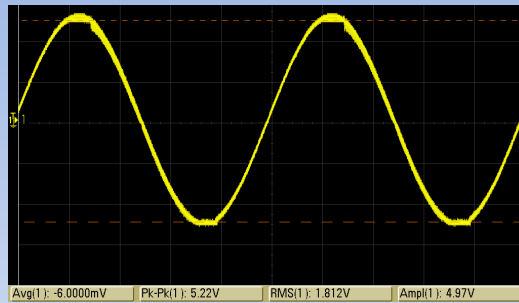


Spot Noise Density Vs. Frequency

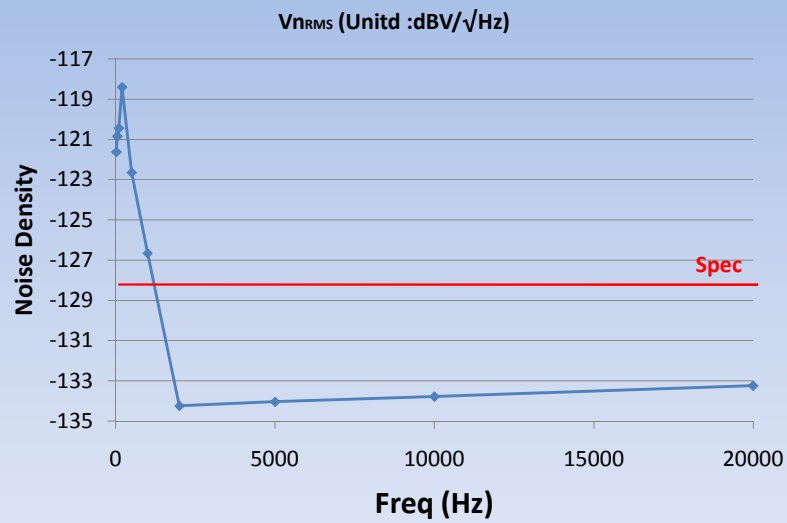

Power Breakdown

- Power measured at 100dB output setting

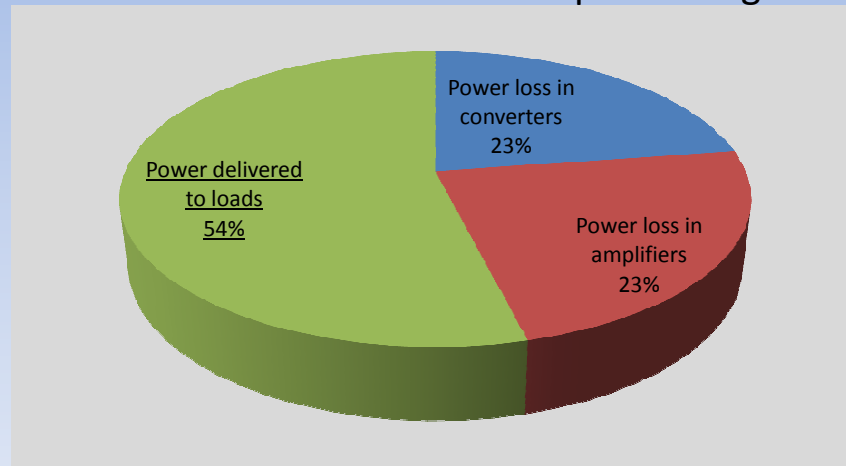

Results Summary

Power Requirements	Measured	Goal
Power Consumption	371mW	< 400mW
Battery Life	101hrs	> 90hrs
Noise Requirements		
THD (10mW output)	.0333% (L) / .0393 % (R)	< 0.1%
THD (100mW output)	.457% (L) / .506% (R)	< 1.0%
Noise Density (output)	See Prev. Slide	< -128dB/VHz
Material Cost		
Amplifier Stage	\$16.01	
Converters	\$19.16	
Jack/Plug	\$1.81	
Overall	\$36.98	< \$40

DC-DC Converter Circuitry

Component name	DigiKey Part #	Manufacturer	Qty.	Cost per unit	Total Cost
LT1615 (Step-up DC-DC converter)	LT1615ES5#TRMPBFCT-ND	Linear	1	\$ 3.330	\$ 3.330
LTC3429 (Step-up DC-DC converter)	LTC3429ES6#TRMPBFCT-ND	Linear	1	\$ 3.667	\$ 3.667
LT1617 (Inverting DC-DC converter)	LT1617ES5#TRMPBFCT-ND	Linear	1	\$ 3.330	\$ 3.330
BAT47 (Schottky Diode)	497-3773-1-ND	STMicroelectronics	3	\$ 0.460	\$ 1.380
1/4 W Carbon Film Resistor	CF1/4(Value)%5RCT-ND	Stackpole Electronics, Inc.	4	\$ 0.019	\$ 0.076
1/4 W Metal Film Resistor	(Value)XBK-ND	Yageo	2	\$ 0.037	\$ 0.074
Radial Aluminum Electrolytic Capacitor					
10 uF	P5567-ND	Panasonic	2	\$ 0.077	\$ 0.154
330 uF	P5573-ND	Panasonic	1	\$ 0.260	\$ 0.260
470 uF	P5585-ND	Panasonic	1	\$ 0.492	\$ 0.492
Ceramic Chip Capacitor					
4.7 pF	478-1159-1-ND	AVX	1	\$ 0.124	\$ 0.124
100 pF	399-1122-1-ND	Kemet	1	\$ 0.057	\$ 0.057
100 nF	399-1096-1-ND	Kemet	6	\$ 0.012	\$ 0.070
220 nF	399-1103-1-ND	Kemet	1	\$ 0.183	\$ 0.183
Inductor 10uH	308-1311-1-ND	SUMIDA	2	\$ 1.490	\$ 2.980
Inductor 4.7uH	308-1317-1-ND	SUMIDA	2	\$ 1.490	\$ 2.980

Total Cost of Converter: \$19.16

Amplifier Circuitry

Component name	DigiKey Part #	Manufacturer	Qty.	Cost per unit	Total Cost
MAX4332	MAX4332ESA+-ND	Maxim	2	\$ 3.450	\$ 6.900
BAT46	497-5559-1-ND	STMicroelectronics	5	\$ 0.211	\$ 1.056
1N4148	568-1360-1-ND	NXP Semiconductors	5	\$ 0.010	\$ 0.052
PBSS4350X (NPN transistor)	568-4159-1-ND	NXP Semiconductors	4	\$ 0.450	\$ 1.800
PBSS5350X (PNP transistor)	568-4170-1-ND	NXP Semiconductors	4	\$ 0.600	\$ 2.400
2N5551RLRAGOSCT-ND (NPN Transistor)	2N5551RLRAGOSCT-ND	ON Semiconductor	2	\$ 0.185	\$ 0.370
Radial Aluminum Electrolytic Capacitor					
1 uF	P5563-ND	Panasonic	1	\$ 0.077	\$ 0.077
4.7 uF	P5566-ND	Panasonic	1	\$ 0.069	\$ 0.069
10 uF	P5567-ND	Panasonic	2	\$ 0.077	\$ 0.154
22 uF	P5568-ND	Panasonic	2	\$ 0.068	\$ 0.136
470 uF	P5585-ND	Panasonic	2	\$ 0.492	\$ 0.984
Ceramic Chip Capacitor					
100 nF	399-1096-1-ND	Kemet	3	\$ 0.012	\$ 0.035
1/4 W Metal Film Resistor	(Value)XBK-ND	Yageo	12	\$ 0.037	\$ 0.444
1/4 W Carbon Film Resistor	CF1/4(Value)%5RCT-ND	Stackpole Electronics, Inc.	4	\$ 0.019	\$ 0.076
10KΩ Pot	P2U4103-ND	Panasonic	1	\$ 1.460	\$ 1.460

Total Cost of Amplifier: \$16.01

Conclusion

- Better dc/dc converters or design to avoid poor power efficiency at low voltages